

Time : 2 Hours

Max. Marks : 40

- 1 (a) The UPFC linearised power equations are written as

$$[f(x)] = [J] [\Delta X]$$

where $[f(x)]$ is mismatch vector, $[J]$ is Jacobian and $[\Delta X]$ is the correction vector. The UPFC is used for the following modes of operation:

- (i) Real and Reactive power flow control on the line and voltage control at the UPFC bus;
- (i.i) Only for real and reactive power flow control with magnitude of the shunt converter voltage fixed.

What are mismatch and correction vectors in each of the above two cases? (5)

- (b) The control region of the attainable real power P and receiving-end reactive power demand Q with a UPFC controlled transmission line is expressed as:

$$\{P(\delta, P) - P_0(\delta)\}^2 + \{Q(\delta, P) - Q_0(\delta)\}^2 = \left\{ \frac{V V_{pqrmax}}{X} \right\}^2$$

Derive the above equation for a transmission line assuming $V_s = V_r = V$ and line reactance $= X$. (5)

- 2 (a) Explain the principle of operation of a typical two converter Interline Power Flow Controller (IPFC). Considering system 1 as prime system, explain the constraints on the operation of the converter 2. (5)

- (b) "TCBR is used for enhancing transient stability of a power system". Explain with the help of equal-area criterion of stability the transient

stability enhancement in terms of "stability margin".
Explain control scheme of the TCBR.

(5)

- 3 (a) Explain the principle of operation of "NGH-SSR Damping Scheme". The TCSC is used for regulating power flow on a line. What is the difference in the operation of TCSC as compared to NGH-SSR Damping scheme? Is TCSC SSR neutral? Explain

(5)

- (b) Draw a neat circuit diagram of 3-phase TCPAR. What are the merits of using 'ternary proportioned winding sections' as compared 'equal winding' sections.

(5)

- 4 (a) The current rating of the FC is 1 pu and that of TCR is 0.5 pu of an SVC. Sketch the V-I characteristic of the SVC.

(2)

- (b) What are the parameters of the power semiconductor devices which determine power dissipation when used in converters?

(2)

- (c) A TCSC consists of a fixed capacitor (capacitive reactance = 1.33Ω) and TCR (inductive reactance = 2Ω). Sketch the variation of TCSC reactance over the complete operating range.

(2)

- (d) What is the difference between "internal" and "external" controls of the FACTS devices?

(2)

- (e) A STATCOM is installed at the mid-point of a transmission line. Compute the power transmitted if $V_s = 1$ pu, $V_r = 1$ pu, $V_m = 0.95$ pu and line reactance $X = 1$ pu. Assume $\delta = 60^\circ$.

(2)