

ELECTRICAL ENGINEERING DEPARTMENT

EEL202 Circuit Theory

Major

1 - 3 pm

30/11/2006

MM: 45

Q1. Using Talbot's method, test if $Z(s) = \frac{36s^4 + 30s^3 + 24s^2 + 5s + 1}{18s^3 + 6s^2 + 3s}$ is PR. If yes then realize it. (9)

Q2. Find the minimum real part of the function $Z(s) = \frac{6s^2 + 19s + 18}{s^2 + s + 10}$. Is the minimum real part of $Z(s)$ same as that of its inverse? Is the frequency at which the real part of $Z(s)$ is minimum, the same as that for its inverse? (6)

Q3. Given that $\text{Re}\{F(j\omega)\} = \frac{\omega^4 + 21\omega^2}{\omega^4 + 17\omega^2 + 16}$. Determine a realizable $F(s)$. (5)

Q4. Determine the scattering parameters of the cascaded lattice network shown in Fig.1. Also find the insertion loss of this network. (6)

Q5. Synthesize the voltage transfer function $T(s) = \frac{V_2(s)}{V_1(s)} = \frac{K2s}{s^3 + 2s^2 + 2s + 1}$ in two different ways using the transmission zeros method. Also find the realized value of K . (7)

Q6. Synthesize $Z(s) = \frac{s^2 + s + 1}{s^3 + 5s^2 + 2s + 1}$ using the Brune's method. (7)

Q7. Obtain y-parameters of the twin-T network in Fig.2 using bisection theorem. (5)

-x-x-x- All the best -x-x-x-

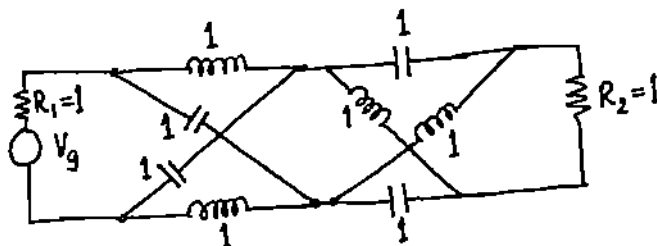


Fig.1

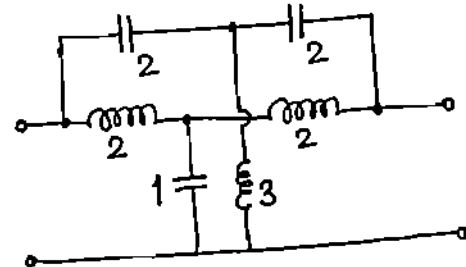


Fig.2