

MAJOR
EEL324 Digital Hardware Design

Time: 2 Hour

Max. Marks: 40

N. B.:- This is **open notes examination**. **Transfer** of notes to each other is strictly **prohibited**. Write in the answer script.

Q 1:- For the following state assignment and transition table (Of synchronous sequential machine) construct excitation and output maps for **D flip-flop**. Draw the diagram (using D flip-flop) of resulting circuit.

(4)

y_1y_2	$(y_1y_2)^+, z$	
	$x=0$	$x=1$
A→00	01,0	00,0
B→01	01,0	10,0
D→11	01,0	10,1
C→10	11,0	00,0

Q 2:- Draw flow table for the asynchronous circuit that has two inputs (x and y) and an output (z). If x and y agree ($x = y$), then $z = x = y$. Otherwise z retains the last value at which x and y agreed.

(3)

Q3 (a):- Why and how hardware-software co-design implemented? In your words (Less than **60** words **strictly**) highlight the main points.

(b):- In your words discuss **issues** and their **remedies** in energy efficient design methodology.

(Preferably use tabular form with less than 60 words)

(3+3)

Q4: If there are two functions ' f ' and ' g ' as given below:

$$f = x + y \cdot z'$$

$$g = y + z \cdot r$$

(where z' is complement of z)

The variable ordering is $x < y < z < r$. Compute the function $f \cdot g$ using **ITE** operator. Show all steps and ROBDD's of original and resultant function.

(5)

Q5 (a): Sketch schematics for the following constructs. Unless specified other wise, assume signals of the type **std_logic** or **std_logic_vector** of appropriate size.

```
IF a OR b THEN
    Z <= X;
ELSEIF a AND b THEN
    Z <= NOT X;
ELSE
    Z <= Y;
ENDIF;
```

(b): Write a short VHDL description of a positive edge-triggered 'D' flip-flop using a VHDL process.

(2+3)

Q6: A Moore machine has two inputs x and y , and an output z . The machine starts in an *idle* state in which $z = 0$. When in the idle state, it processes its inputs as follows:

xy	action
00	remain idle
01	assert z for 1 clock cycle, and then return idle
10	assert z for 2 clock cycles, and then return idle
11	assert z for 3 clock cycles, and then return idle

When the machine is not in the **idle state**, it disregards the value of the inputs. Draw the state transition diagram for this machine using the least number of states, and implement using 1-hot encoding.

(6)

Q7: If the collision vector of nonlinear pipeline is as:

Collision vector: $C = \{1\ 0\ 1\ 1\ 0\ 0\ 0\ 1\}$

Find greedy cycles, cycles and MAL after drawing the state diagram. (Right most is smallest element of vector)

(4)

Q8 (a):- For the following Petri net (as given in Fig. 1.3.5), construct the coverability-tree. Also if possible draw reachability-tree for the same Petri net.

(4)

 


Fig.1.3.5 Petri net with initial setting $\langle 0,1,0,0 \rangle$.

(b):- Highlight main features of Petri net as compared to others. It's strong and weak points in **less than 30 words only**.

(3)