

Q1.

 


Fig1 shows a gate implementation of a 4 input MUX. Realize the mux with (a) DOMINO CMOS and (b) Static CMOS. Compare their performance in terms of delay and power dissipation.

(5 + 5 + 2) = 12

Q2.

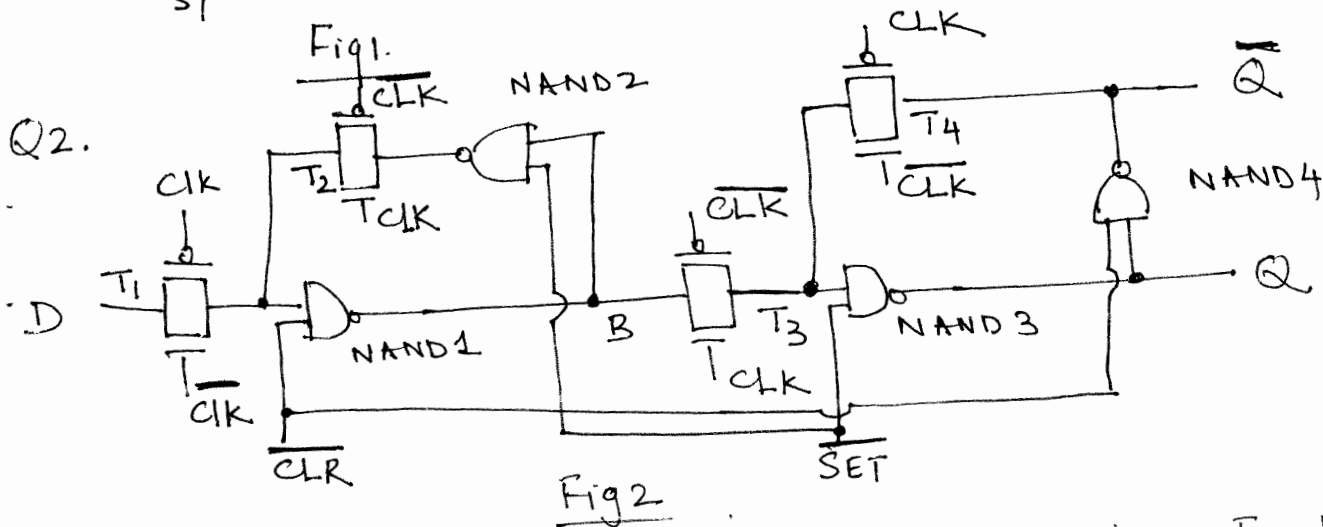


Fig2 shows an edge-triggered D flipflop. Find (i) setup time (ii) hold time and propagation delay time of the flipflop. Draw the wave form of CLK and Q.

(2 + 2 + 2 + 1) = 7

Q3.

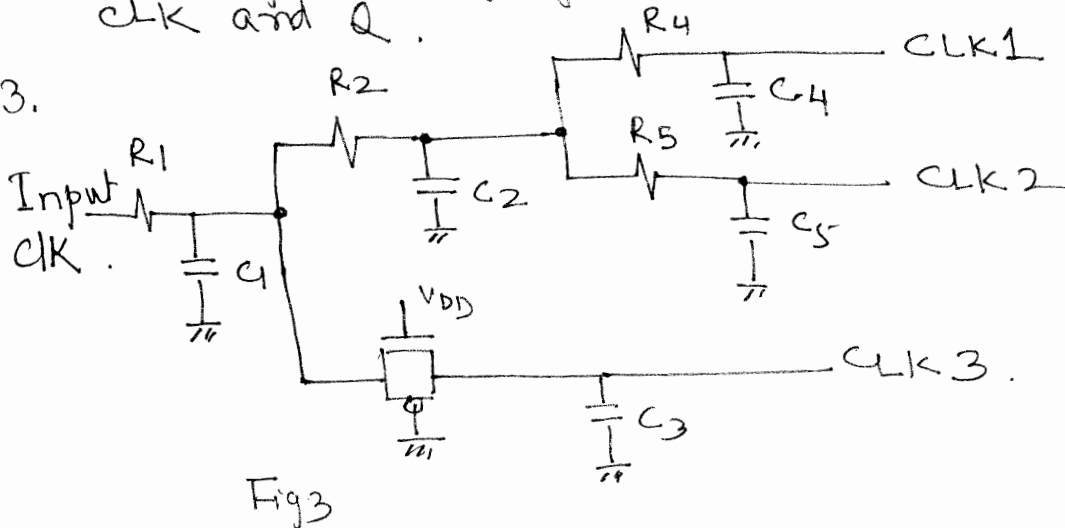


Fig 3 shows a clock distribution network.

(a) Write the expressions for the time constants associated with CLK1, CLK2 & CLK3

(b) If  $R_1 = R_2 = R_4 = R_5 = R$  and  $C_1 = C_2 = C_3 = C_4 = C_5 = C$  what value of  $R_3$  is required to balance delays of CLK1, CLK2 and CLK3

(c) For  $R = 750 \Omega$ ,  $C = 2000 \text{ fF}$  what (W/L) is required for the transmission gate to eliminate skew? Given:  $K_n' = 80 \mu\text{A/V}^2$ ,  $K_p' = 27 \mu\text{A/V}^2$  and  $V_{DD} = 1.8 \text{ V}$ .

Q4 (a)

 


Fig 4

Consider the binary tree shown in Fig 4. Apply Kernighan-Lin Algorithm to this graph. The initial partition is given all the leaves are in one partition and the rest of the nodes are in the other partition  $(3 + 2 + 3)$ .

(b) 

1	2	3	4
---	---	---	---

3	1	2	4
---	---	---	---

-- 2

A channel with a side pin is shown. Draw the HCG and VCG of the channel.  $(4 + 4)$ .