

Major Examination

Fundamental of RF Electronics CRL-713


Time: 2 Hour

Maxm. Marks 30

1. The small signal equivalent circuit of the output stage of an OPAMP is shown below. The biasing collector current of transistor Q_2 is $165 \mu\text{A}$, and biasing collector current of transistor Q_1 is $16 \mu\text{A}$. Use a simple (g_m , r_π) model of each transistor to find the output impedance R_O of this circuit. The transistor Q_3 is sourcing the current of 5 mA . The pnp transistors are characterized with an early voltage of 50 V , β of 50 , and the npn transistors have β of 200 and early voltage of 125 Volts .

(Hint: first find the small signal resistance between A, and B)

10 Marks

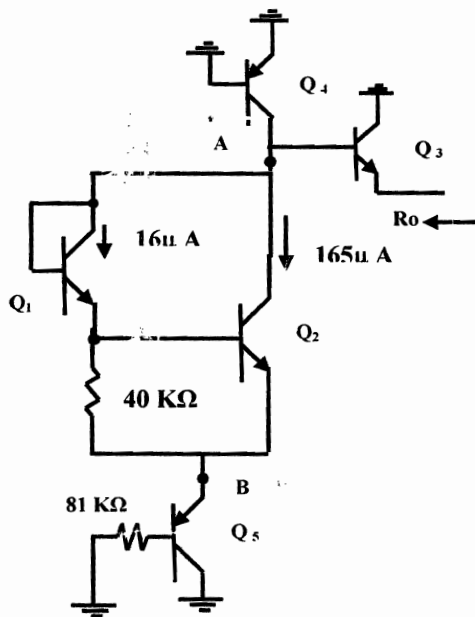

- Q2. Find the autocorrelation function of the signal $g(t) = e^{-at} u(t)$ and validate the Parseval's Theorem by computing the signal energy in the time and frequency domain.

3Marks

- Q3. Let $g(t)$ is a base band signal band limited to $B \text{ Hz}$. It is double side band, b suppressed carrier modulated using the carrier $\cos \omega_c t$. The frequency ω_c is chosen such that $\omega_c \gg 2\pi B$. Show that the energy of the modulated signal is half the modulating signal $g(t)$.

5 Marks

- Q4. Two base band signals $m_1(t)$ and $m_2(t)$ are transmitted using the QAM technique. The output of the modulator is $\phi_{AM}(t) = m_1(t) \cos \omega_c t + m_2(t) \sin \omega_c t$. At the receiver side the locally generated carrier has a frequency error of $\Delta\omega$ and phase error of δ . Show that the output of the receiver after passing through the band pass filter is: $m_1(t) \cos [\Delta\omega t + \delta] - m_2(t) \sin [\Delta\omega t + \delta]$ rather than $m_1(t)$.

2 Marks

- Q5. Draw the signal flow graph for solving the simultaneous equations given below: 7 Marks (hint: express eq. 1,2,3 in terms of X_1, X_2, X_3 , respectively then draw the signal flow graph)

7 Marks

$$a_{10} X_0 + a_{11} X_1 + a_{12} X_2 + a_{13} X_3 = 0$$

$$a_{20} X_0 + a_{21} X_1 + a_{22} X_2 + a_{23} X_3 = 0$$

$$a_{30} X_0 + a_{31} X_1 + a_{32} X_2 + a_{33} X_3 = 0$$

- Q6. A certain two port network is measured to have the scattering parameters as: $S_{11} = 0.1 \angle 0^\circ$, $S_{12} = 0.8 \angle 90^\circ$, $S_{21} = 0.8 \angle 90^\circ$ and $S_{22} = 0.2 \angle 0^\circ$. Determine whether the network is reciprocal or lossless. If a short circuit is placed on port 2, what will be resulting return loss at port 1.

3 Marks