

EEL 102 - Principles of Electrical Engineering

Major Test

May 1, 2009

PART 1

Answers to part 1 should be marked CLEARLY in the answer book. Each question carries 2.5 marks and there is only one correct option. Wrong answers will carry a penalty of 1 mark. Part 1 must be attempted before attempting Part 2

1. The number of parallel paths in a lap wound armature is equal to
 - (a) Two
 - (b) the number of poles
 - (c) twice the number of poles
 - (d) none of these
2. Interpoles are added in a DC machine in order to counter —— effect of the armature reaction.
 - (a) self magnetising
 - (b) demagnetising
 - (c) cross magnetising
 - (d) remagnetising
3. A two winding transducer essentially produces a torque proportional to the product of
 - (a) two currents
 - (b) two voltages
 - (c) a current and a voltage
 - (d) none of these
4. Which of the following is not required for the operation of a self-excited DC generator
 - (a) Residual magnetism in the field winding
 - (b) Polarity of armature winding should aid field build-up in shunt winding
 - (c) a separate field excitation
 - (d) All three conditions are required
5. Of the following the reason for a DC generator producing a DC voltage at the output terminals rather than an AC voltage is
 - (a) armature reaction
 - (b) *commutation
 - (c) saturation of magnetic field
 - (d) cumulative coupling
6. A transformer is so designed that primary and secondary coils have
 - (a) high leakage reactance
 - (b) large resistance
 - (c) coupling coefficient close to unity
 - (d) good electrical coupling

PART 2

1. Draw the equivalent circuit of a two winding non-ideal transformer and indicate the significance by each parameter in the circuit. ... (7)
2. A 1200/240 V rms transformer has an impedance $60\angle 30^\circ \Omega$ connected in series on the high voltage side. If the transformer is connected to a load of $0.8\angle 10^\circ \Omega$ on the low voltage side, determine the primary and secondary currents and the average power consumed by the load when the transformer is connected to 1200 V rms supply. ...(6)
3. Three equal impedances, $60 + j30 \Omega$ each are delta connected to a 230 V rms, three phase circuit. Another three equal impedances, $40 + j10 \Omega$ each, are wye connected across the same circuit at the same points. Determine :
 - (a) the line current ... (2)
 - (b) the total complex power supplied to the two loads ... (2)
 - (c) the power factor of the two loads combined ... (1)
4. A non-ideal opamp has an open loop gain of 10^5 . It is connected in a voltage follower configuration. Assume an input resistance of $10k \Omega$ and an output resistance of 100Ω .
 - (a) Draw the equivalent circuit for a non-ideal opamp. ...(2)
 - (b) Find the voltage gain achieved the circuit described above using this model. ...(5)