

Max Time 2 hours

Max Marks 60

Answer all Questions. Answer to the point with neat diagrams where needed

Q-1 (a) Explain using suitable diagram why sensitivity and resolution are contradictory requirements in a wire wound potentiometer? (2 marks)

(b) How using a conducting paste modifies the limitation? (2 marks)

Q-2 Explain with suitable diagram

a) Working of ultrasonic flow meter (3 marks)

b) Working of turbine flow meter (3 marks)

c) Compare four important performance differences of (a) & (b), w.r.t. threshold detection, span, type of fluid, accuracy. (2 marks)

Q-3 a) Give a neat diagram of smart sensor. Tabulate the main differences between a conventional and smart sensor? (3 marks)

b) What additional features does an intelligent sensor have over smart sensor? (3 marks)

Q-4 a) Draw the diagram of 4 wire RTD. (2 marks)

b) Explain :-

(1) How a 4 wire RTD reduces lead length error as compared to a 2 wire RTD. (2 marks)

(2) How a 4 wire RTD induces less noise in bridge output detection compared to a 2-wire RTD? (2 marks)


Q-5 a) For a fully active strain gauge bridge, derive the bridge o/p voltage  $e_0$  in terms of strain  $\epsilon$ , Gauge factor  $G$  and excitation voltage  $E$ . (4 marks)

b) If  $R_{\text{gage}}=250\Omega$ ,  $G=2$  and  $E=12V$ , Calculate  $e_0$  for  $\epsilon=10^{-4}$ . (2 marks)

Q-6 Draw circuit diagram of half wave precision rectifier and plot the o/p voltage  $V_0$  Vs time if the input voltage  $V_{\text{in}}$  is  $V_{\text{in}}=2.5 \sin(250\pi t)$  volts. (4 marks)


Q-7 Explain working of synchronous detector with the help of suitable block diagram and waveforms. (4 marks)

Q-8 The angular motion of a robotic arm is to be measured by a semicircular potentiometer as shown in figure. The initial position of robotic arm is  $100^\circ$  and maximum possible rotation is  $200^\circ$  and it is to move & measure  $\theta=\pm 90^\circ$  about initial position. The output voltage is required to be zero at initial position the total span of output voltage is  $\pm 9V$ . The rotary arm length is 50mm, wire diameter of  $50\mu\text{m}$ .

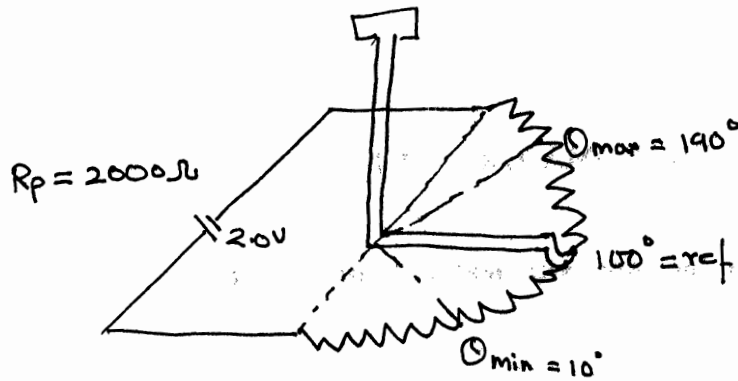

- Give complete circuit diagram to achieve the above. (2 marks)
- Using loading error  $< 1\%$ , calculate all resistances values in circuit. (2 marks)
- Calculate angular resolution in degrees. (2 marks)

Q-9

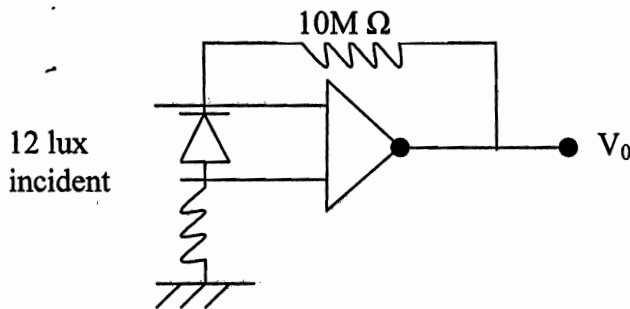

Photodiode sensitivity is  $0.3 \text{ nA per lux}$ . Calculate the voltage output? (2 marks)

- Q-10 A strain gauge for load cell application has to give a  $20 \text{ mV}$  calibrated response from a strain of  $\epsilon = 10^{-3}$  in a full bridge configuration. If the gauge factor is 10 &  $R = 150 \Omega$ , the supply voltage varies from 8 volts to 10V, Find the min value of sensitivity adjustment potentiometer? (4 marks)

- Q-11 The capacitance in pF of a rotary capacitance transducer varies as

$$C = (100 + 0.2\theta) \text{ with } \theta \text{ in deg.} \quad \theta \rightarrow 0^\circ \text{ to } 100^\circ.$$

It is proposed to measure the angle by using suitable conditioning method.

- What inductor value should be chosen to give resonant frequency =  $1 \text{ Mhz}$  (1 marks)
  - What choice of reference oscillator frequency will you make and plot  $\Delta f$  Vs  $\theta$  for this choice? (2 marks)
  - What is the required resolution of frequency counter to read  $\Delta\theta = 1^\circ$ ? (2 marks)
- Q-12 Explain with the help of neat block diagram the basic principle of detection of a chemical substance using piezo electric effect. Draw the block diagram for electron conditioning that can be used for above? (5 marks)