

ELECTRICAL ENGINEERING DEPARTMENT

EE734 MOS LSI


Date: December 1, 2006

Time: 1:00PM to 3:00PM

- Q1. a) We discussed about the address multiplexing in a DRAM. Draw a block diagrammatic set up for generating the relevant Row Address and Column Address signals/clocks to carry out READ and WRITE operations after a Address Transition is detected and the memory operation is enabled.
- b) In order to reduce the overhead on address decoding one of the schemes used is to detect the address transmission. This is useful in page mode of operation when the x-address remains the same while the y address is changed. Propose a scheme that can be used to detect the address transition and give its CMOS realization. Hint: Detection of address transition means detection of non identical values at successive clock instants.

— (20)

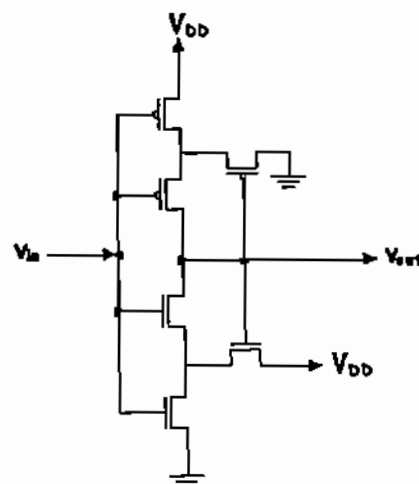
- Q2. a) You are to design a six transistor CMOS SRAM cell. In designing the W/L ratios of the various transistors enunciate the criterion to be used and explain.
- b) Draw the transfer characteristics of the CMOS logic circuit shown below and identify its function.
- c) We discussed dynamic and static combinational circuits in the class, write a few words on static and dynamic sequential circuits with examples.
- c) Design a CMOS gate that gives at the output $\overline{ABC} + \overline{ABD}$ and identify its logical effort.



— (20)

- Q3. For the combinational circuit find the input test vector to detect s-a-0 and s-a-1 faults at the node A.

— (10)

 

BEST OF LUCK

