

Department of Electrical Engineering IIT Delhi

SEL842

Power Conditioners

Max Marks 50

Major Test (03/05/09)

Time 120 min


Q1. (a) Give layout of a series cascaded thyristorised 12-pulse converter and describe its operation. [4]

(b) The above converter is fed from a 380V, 50Hz supply with $L_s = 0$ has a continuous ripple free load on its dc bus having $R_{dc} = 50\Omega$. 6-pulse converter with $\lambda-\lambda$ input has $\alpha = 30^\circ$ and the other has $\alpha = 45^\circ$.

(c) Draw the resultant current waveform at primary input of the 12-pulse converter transformer. [4]

(ii) obtain the amplitude of fundamental component of resultant primary input current in phase A and phase angle. [2]

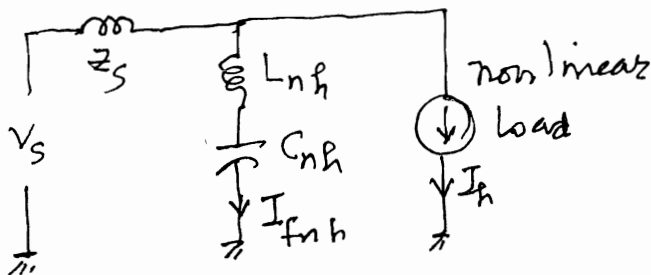Q2. A power network is having the following filter configuration shown in the figure. Each filter is tuned



to resonant frequency ω_h and the harmonic frequency order due to non-linear load be h (5, 7, 11, 13...). Due to detuning of the filter parameters $\omega_h \neq h$.

Derive the expression for per unit impedance shown by the detuned ω_h filter to the h^{th} harmonic current at fundamental base impedance Z_b as $\frac{S_b}{Q_{rh}} \frac{(h^2 - \omega_h^2)}{h(\omega_h^2 - 1)}$,

where S_b is the fundamental base VA of the system and Q_{rh} is the fundamental VAR loading of the ω_h filter. Give layout for 5th, 7th, 11th and 13th filter. [7+5]

Q3. Give layout of a parallel hybrid active filter for 5th and 7th harmonics. Describe its operation on the basis of use of SRF controller for parallel hybrid active filter induction variation with mistuned passive filter configuration. [5+5]

Q4. (a) Draw the layout of a half bridge converter/inverter based 1-phase UPS, which has battery charging by stepup/down chopper. Give details of the devices. Explain the rectifier operation [5]

(b) Draw the layout of isolated dual redundant UPS system with double throw switch. Explain its operation in preferred on line mode of UPS operation. Give the necessary protection. [5]

Q5. Explain the operating principle of an UPFC. Derive expressions for the transmitted power P and the reactive power at the receiving end Q_r as a function of supply and receiving end voltages $V_s \angle \delta^\circ$, $V_r \angle 0^\circ$, transmission line reactance X and UPFC voltage $V_{pq} \angle \phi$. Where ϕ is measured with respect to $V_s \angle \delta$.

When the transmission line has a series capacitor compensation with $X_c = \frac{X}{4}$, obtain P and Q_r for $\delta = 45^\circ$. Get $V_{pq} \angle \phi$ for transmission line operating with UPFC for corresponding P and Q_r as achieved with series capacitor compensator. [3+3+4]