

**Electrical Engineering Department**  
**EEL404/EEL894 Flexible AC Transmission System**  
**Major Test**

Time allowed- 2 hour

Maximum Marks- 40


Answer all questions

Q.1

- i. Draw the phasor diagram of a type-1 converter system and explain how we can regulate both magnitude and phase angle of the output voltage.
- ii. In case of a Type-2 converters based SSSC the magnitude of voltage injection is varied by making the voltage injection angle with respect to the line current  
a.  $=90^\circ$  b.  $\neq 90^\circ$  (in a small range) c.  $0^\circ$  d. None of these.
- iii. Will a SSSC be SSR neutral even when the DC capacitor voltage fluctuates?  
a. Yes b. No
- iv. An UPFC can regulate \_\_\_\_\_ flow in the transmission line.  
a. real power b. reactive power c. both real and reactive power
- v. PLL is used for measuring \_\_\_\_\_.
- vi. In case of a STATCOM supplying reactive power to the bus, the maximum power occurs at what power angle ( $\delta$ )?  
a.  $>90^\circ$  b.  $<90^\circ$  c.  $90^\circ$  d. can occur at any angle
- vii. Transport delay for a 12 pulse converter is \_\_\_\_\_ when the time period is "T".
- viii. If the ESCR of the system at the SVC bus is increased then the response time of SVC will  
a. decrease b. increase c. remains same
- ix. In case of a TCSC the susceptance of reactance is \_\_\_\_\_ capacitance.  
a. greater then b. less then c. equal d. can not be predicted
- x. The effective capacitance for a STATCOM with a capacitor 'C' is  
a.  $C/k^2$  b.  $k^2C$  c.  $kC$  d.  $C/k$

Marks = 10

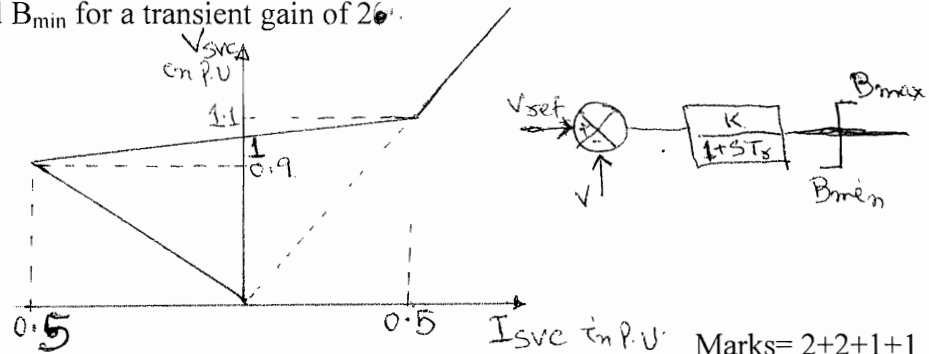Q.2 The steady state SVC characteristics and the corresponding voltage control loop are given below. Find out 'K', ' $T_r$ ',  $B_{\max}$  and  $B_{\min}$  for a transient gain of 20.



Marks= 2+2+1+1

Q.3 Draw the control block diagram of a Type-2 SSSC. Explain how we can regulate the magnitude of injected voltage. If the injected voltage is increased by 1% what will be the phase difference between the line current and the injected voltage at steady state. Marks= 4+2+1

Q.4 Derive from the basic the load injection model of an UPFC.

Marks = 7

Q.5 A SSSC is used for regulating the real power flow in a transmission line. Compute the value of transmitted real power, current and rating of SSSC for  $V_S=V_R=1$  pu;  $X=1.05$  pu and  $V_q=0.85$  pu for a power angle ( $\delta$ ) of  $45^\circ$ . Marks = 5+3+2